



Static timing analysis

VLSI CAD

Compiled by Oleg Venger


Representation of combinational circuits

  - Timing graph: $G(V, E)$ where
- V includes all terminals of cells
- E has two types of elements:
 - **Timing arcs:**
 - Combinational cell:
 - from each input to output – propagation delay
 - Sequential cell:
 - From clock input to output(s) – propagation delay
 - From clock input to data input – setup, hold checks
 - **Interconnect delays:** connect cell output to the inputs of its fanout gates



Background

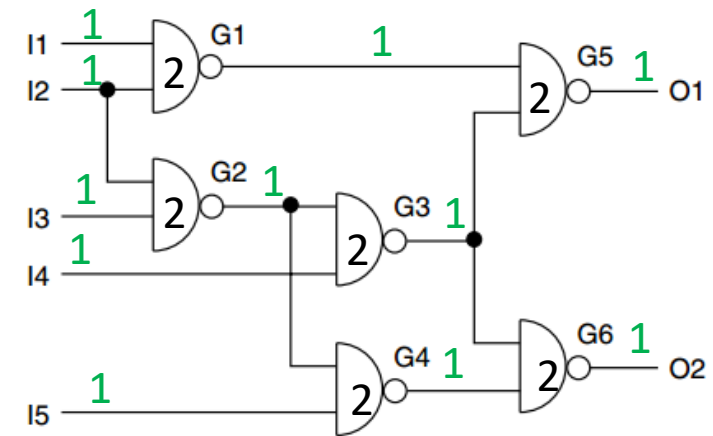
- Netlist is represented as Directed Acyclic Graph (DAG) – timing graph
- Delay values associated with edges of timing graph
- Timing information is associated with topological paths:
 - Start point
 - End point
 - Path delay
- Total path delay is the sum of stage delays (cell and net delays) along the path
- Maximum path delay through a combinational block defines the speed of the circuit



What is max path delay for this circuit?

Delay parameters

 - t_r : rise transition time
 - From output crossing 0.1 VDD to 0.9 VDD
- t_f : fall transition time
 - From output crossing 0.9 VDD to 0.1 VDD
- t_{pdr} : rising propagation delay
 - From input crossing VDD/2 to rising output crossing VDD/2
- t_{pdf} : falling propagation delay
 - From input crossing VDD/2 to falling output crossing VDD/2
- Can t_{pd} be negative?



Inverter timing response

Gate delay models

- Standard cell delays are pre-characterized for various capacitive loads C_L and input transition time τ_{in}
- Some commonly used cell delay models:
 - Look-up tables with each entry in the table corresponding to the delay under different capacitive loads and different input transition times
 - $D = k_1 + C_L k_2$. Where k_1 - intrinsic delay. k_2 - drive strength
 - $D = \alpha \tau_{in} + \beta C_L + \gamma \tau_{in} C_L + \delta$
 - Etc
- After calculation, delay is scaled by the operating conditions:
 - $FinalDelay = CalculatedDelay * K_{voltage} * K_{temperature} * K_{process}$

Interconnect delay: wire load model

- Net delay results from the need for charging/discharging all the parasitics of a given net. It is a function of net capacitance and net resistance
- Wire load model (pre-layout)
 - Net length is a function of net fanout and block area
 - For a given block area, averages of R and C are estimated for different fanouts
 - Net delay is calculated simply as $R * C$


Capacitance as a function of fanout :

1	0.015
2	0.030
3	0.046

Resistance as a function of fanout :

1	0.012
2	0.016
3	0.020

 For fanout = 3
Net delay = $0.046 * 0.020$



Interconnect delay: Elmore model


- Pullup or pulldown network modeled as *RC ladder*

- Elmore delay of RC ladder:

- $\tau_{DN} = \sum_{k=1}^N C_k (\sum_{j=1}^k R_j) = \sum_{k=1}^N C_k R = RC \frac{N(N+1)}{2} = rcL^2 \frac{N+1}{2N} \xrightarrow{N \rightarrow \infty} \frac{rcL^2}{2}$



$$R = \frac{r * L}{N}$$

$$C = \frac{c * L}{N}$$

 

Multiple segment nets

  
- The distributed RC delay can be modeled by breaking up a wire into one or more segments and using a lumped π -model for each segment.



Elmore delay: multiple segment nets

- **Resistance-oriented Formula:**
 
$$T_{delay} = \sum_{i \text{ on path}} R_i C_{downstream,i}$$




$$T_{delay,4} = R_1(C_1 + C_2 + C_3 + C_4 + C_5) + R_2(C_2 + C_4 + C_5) + R_4C_4$$

Critical path and slack

- **Arrival time** of a signal is the time elapsed for a signal to arrive at a certain point.
- **Required arrival time** is the latest time at which a signal can arrive without making the clock cycle longer than desired.
- $slack(v) = Req(v) - Arr(v)$
- **Critical path**, defined as the path between an input and an output with the minimal slack
- Slack is constant along the critical path

Arrival time propagation

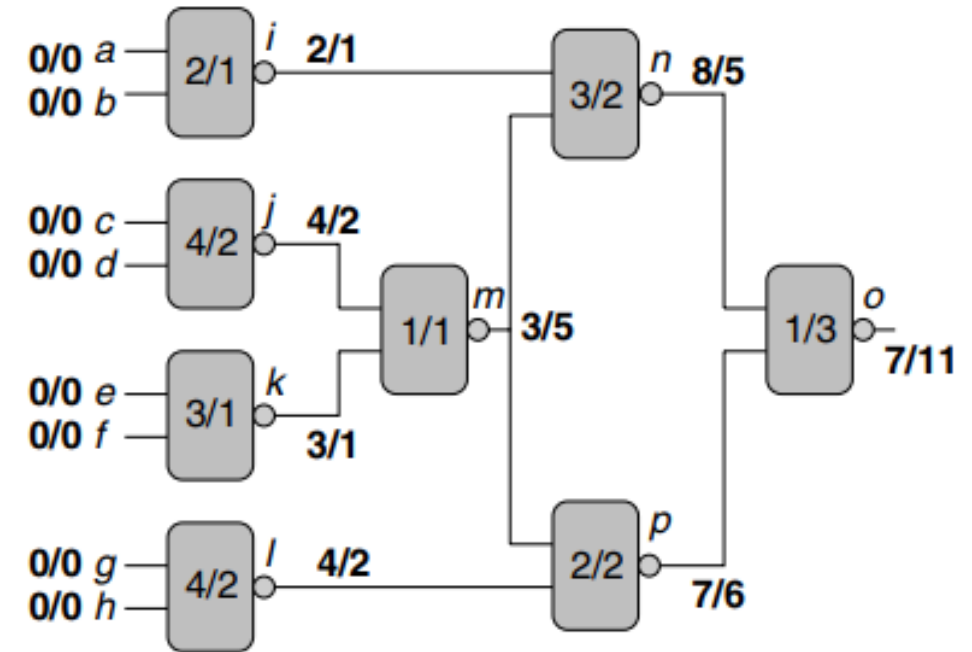
1. **for** each vertex v :
 - $v.num_ready_inputs = 0$
 - **if** v is primary input : add v into *To_Compute* vertex queue
2. **while** *To_Compute* queue is not empty :
 - Get v from *To_Compute* queue
 - **if** v is primary input : $Arrmax(v) = 0$
 - **else** :
 - **for** each input edge (u, v) :
 - $Arrmax(v) = \max(Arrmax(v), Arrmax(u) + d(u, v))$
 - **for** each output edge (v, w) :
 - $w.num_ready_inputs += 1$
 - **if** $w.num_ready_inputs == w.num_inputs$:
 - add vertex w into *To_Compute* queue



Max delay propagation for rise/fall delay (circuit with inverting gates)

Required time propagation

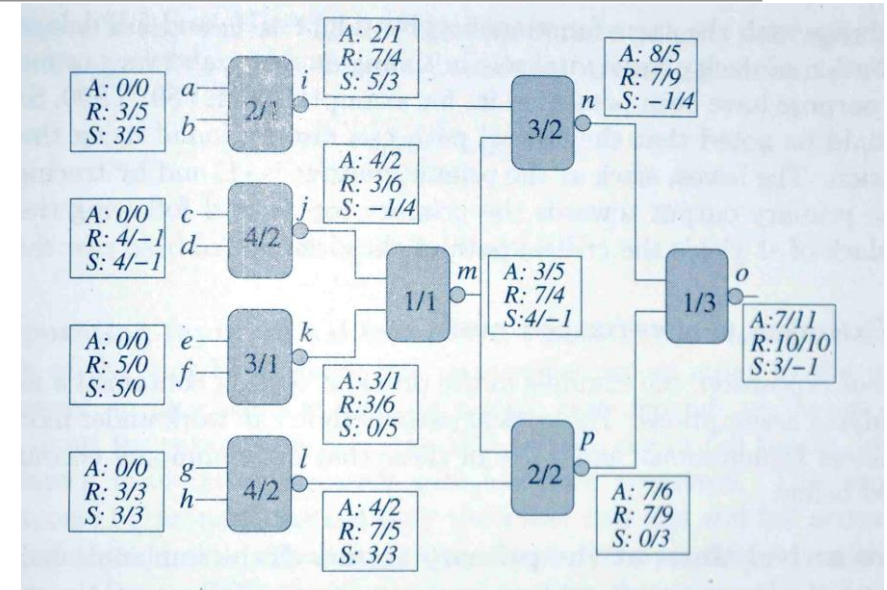1. **for** each vertex v :
 - $v.num_ready_outputs = 0$
 - if v is primary output : add v into *To_Compute* vertex queue
2. **while** *To_Compute* queue is not empty :
 - get v from *To_Compute* queue
 - **if** v is primary output : $Reqmax(v) = T_{clock} - T_{setup}$
 - **else** :
 - **for** each output edge (v, u) :
 - $Reqmax(v) = \min(Reqmax(v), Reqmax(u) - d(v, u))$
 - **for** each input edge (w, v) :
 - $v.num_ready_outputs += 1$
 - **if** $v.num_ready_outputs == v.num_outputs$:
 - add vertex w into *To_Compute* queue




Required time and slack

Extensions of basic algorithm

- Non-zero arrival times at the primary inputs
 - For instance, in hierarchical models
- Minimum delay calculations
 - Propagate earliest arrival time instead of latest
- Minmax delay calculations
 - If the gate delay is specified in terms of an interval $[d_{min}, d_{max}]$
- Non-inverting gates
 - Rise[fall] transition at the output affected by a rise[fall] transition at the input
- Incorporating input signal transition times
 - Propagate arrival time/ transition time pairs
 - Which of two pairs to propagate if $at_1 > at_2$ and $tt_1 < tt_2$?

False paths

 
- Static analysis is fast but leads to **false paths**
- Path of length 4 can never be sensitized (events on this path are not propagated to the output)
 - In fact it can be dynamically sensitizable
- Approaches:
 - Throw out user-specified “non-sensitizable” (false) paths
 - Circuit delay = Length of longest path
 - Too pessimistic



- This leads to functional timing analysis for false paths

Sequential circuits

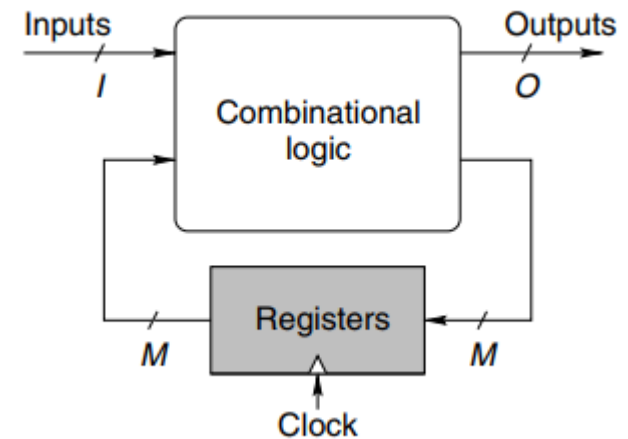- For STA purpose it is possible to represent a sequential circuit as combinational logic with additional inputs and outputs
 - storage elements outputs are considered as primary inputs (PI) to combinational logic
 - storage element inputs are considered as primary outputs (PO) of combinational logic
- STA depends on type of registers
 - Level-clocked latches
 - Edge-triggered flip-flops




Clock skew

- Clock signals do not arrive at all the registers at the same time. This is referred to as 'skew'
- Conventional approach to clock tree synthesis tries to minimize the skew
- Playing with the clock skew might be beneficial:
 - May change the required arrival time for late or early signals
 - Deliberate clock skew is used to reduce dynamic transient current that happens during register switching and could create a significant voltage drop on the power distribution network

Setup and hold times (flip-flop)

 - **Setup time:** amount of time data must be stable at the data pin of flip-flop before the clock capturing edge
- **Hold time:** amount of time data must remain stable at the data pin of flip-flop after the clock capturing edge



STA Constraints

- Main path constraints include:
 - Setup time (Input-to-Reg and Reg-to-Reg paths)
 - Hold time (Input-to-Reg and Reg-to-Reg paths)
 - Input arrival time (Input-to-Reg and Input-to-Output paths)
 - Output required arrival time (Reg-to-Output and Input-to-Output paths)
- Electrical constraints: min and max limits for:
 - Net / Port capacitance
 - Net Transition times

Edge-triggered circuits

- The data input of a register must receive data at least T_{setup} units before the active edge of clock
- The data input of a register must be kept stable for a time of T_{hold} so that data is stored correctly in the flip-flop
- Each register has delay between the time the clock and the data are both available and when it is latched (clock-to-Q delay)
- For timing verification of edge-triggered circuits, it is possible to decompose the circuit into combinational blocks and verify the validity of constraints on each such block independently

Level-clocked circuits

- More complex analysis: combinational blocks are not insulated from each other and multicycle path are possible
- Offer more flexibility both in terms of minimum clock period and minimum amount of memory elements required

Time borrowing

- Level-clocked circuits allow time borrowing i.e. permitting the logic to automatically borrow time from next cycle, thereby reducing the time available for data to arrive for the following cycle

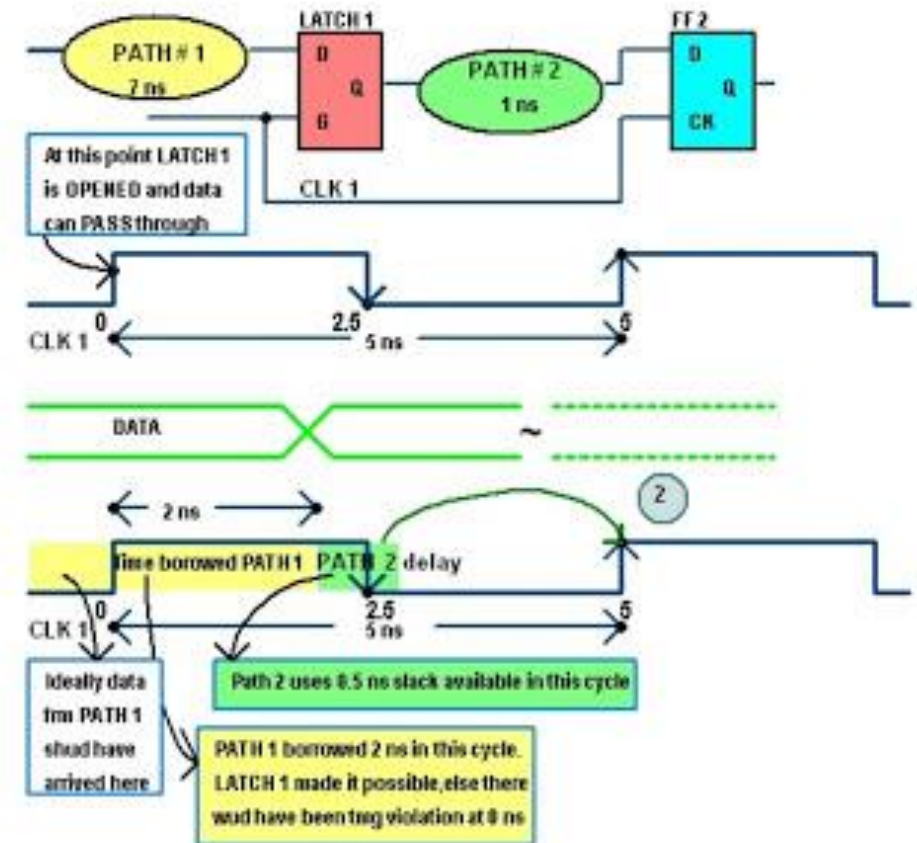


FIG # 2

Statistical STA (SSTA)

- Under true operating conditions, device parameters are perturbed from their nominal values due to various type of variations
- SSTA is an attempt to account for variation while doing timing analysis
- SSTA treats delays not as fixed numbers, but as probability density functions (PDFs), taking the statistical distribution of parametric variations into consideration while analyzing the circuit

Variations classification

- Process variations: result from perturbation in the fabrication process leading to deviations from the nominal values of parameters such as effective channel length, dopant concentration, or interlayer dielectric thickness
 - Inter-die: affect all the devices on the same chip in the same way
 - Intra-die: correspond to variability within single chip
 - Random variations: depict random behavior that can be characterized in terms of distribution. The distribution may either be explicit (built from fabrication line measurements), or implicit (e.g. Gaussian)
 - Systematic variations: show predictable variational trends across the chip, and are caused by known physical phenomena during manufacturing
- Environmental variations: due to changes in the operating environment such as temperature or voltage

Summary

- Static timing analysis applied at various phases of the design
- Linear complexity w.r.t. circuit size
- The closer to final layout the more accurate timing models used
- Accurate timing analysis is very important for circuit optimization

References

- Electronic Design Automation for Integrated Circuits Handbook. EDA for IC Implementation, Circuit Design, and Process Technology. Chapter 6 by Sachin S. Sapatnekar
- Zhou, Shuo, Static timing analysis in VLSI design
- Christiano Forzan. Introduction to Static Timing Analysis
- J.A.N. Rabaey, Digital Integrated Circuits
- N. Weste, D. Harris, CMOS VLSI Design